



C23-EC-302

23130

BOARD DIPLOMA EXAMINATION, (C-23)

MARCH/APRIL—2025

DECE – THIRD SEMESTER EXAMINATION

ELECTRONIC CIRCUITS—I

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :**
- (1) Answer **all** questions.
 - (2) Each question carries **three** marks.
 - (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

- 1. Draw the circuit diagram of half wave rectifier and its output waveform.
- 2. Write the expressions for RMS value and average value (DC value) of voltages and current of full wave bridge rectifier.
- 3. List the factors affecting the operating point.
- 4. Draw the h-model of CE transistor configuration.
- 5. Define the terms Gain in db and bandwidth of an amplifier.
- 6. Draw the practical single-stage transistor CE amplifier.
- 7. Classify power amplifiers based on period of conduction.
- 8. List the merits of negative feedback amplifiers.
- 9. List the advantages of crystal oscillators over other types of oscillators.
- 10. Compare positive and negative feedback.

/23130

1

[Contd...

PART—B

10×5=50

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and the criteria for valuation is the content but not the length of the answer.

- 11.** Explain the working of full wave Bridge rectifier circuit with wave forms.
- 12.** (a) Explain the working of a simple Zener regulator. 5
(b) Explain the concept of DC and AC load lines. 5
- 13.** Explain the fixed bias circuit and list its drawbacks.
- 14.** Explain the working of two-stage transformer coupled amplifier with circuit diagram and also draw its frequency response.
- 15.** Explain the working of complementary symmetry Push-pull power amplifier with circuit diagram.
- 16.** Draw the circuit diagram of double tuned amplifier and explain its operation with frequency response curve.
- 17.** Draw the block diagrams of voltage series, current series, current shunt and voltage shunt feedback amplifiers and compare their characteristics.
- 18.** Explain the working of Hartley oscillator with a circuit diagram.

★ ★ ★